


PLEASE READ: The purpose of this document is to provide examples of pre-lab tasks. The designs, calculations, values, and any other technical aspects of this document will not be suitable for your design.

⊕ Important - rectifier design


1. Current handling of the diode
2. Peak inverse voltage (PIV)

= select a diode that has a reverse breakdown voltage at least 50% greater than expected PIV."

⊕ Design #1 - half wave rectifier

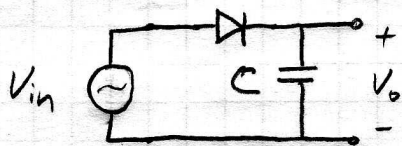

How it operates:

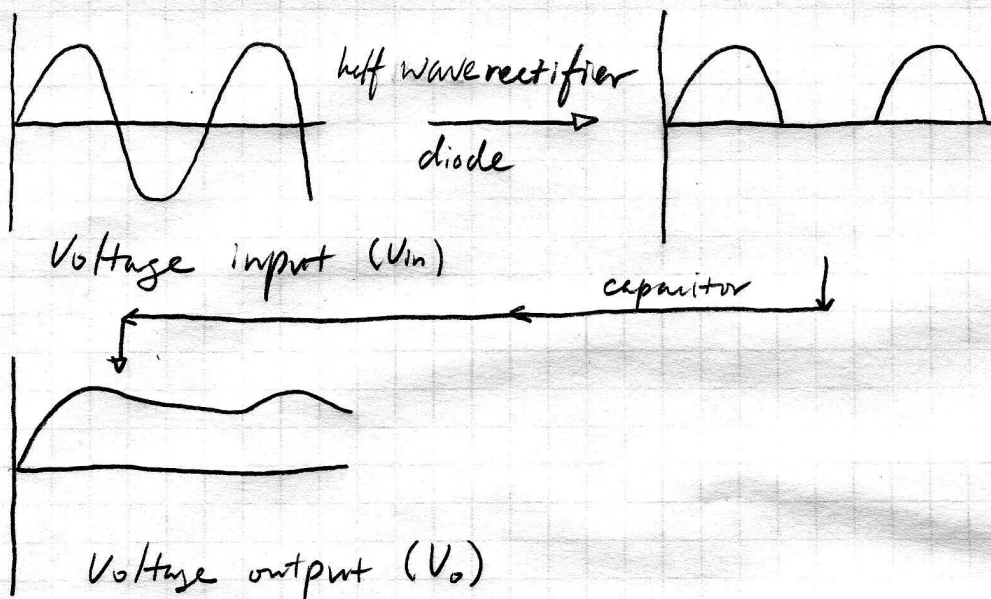

half wave rectifier ripple is given by:

$$V_r = \frac{V_p}{fCR_L}$$

V_r = ripple voltage

V_p = peak voltage

f = frequency

C = capacitance

Given design Spec:


$$V_r < 5 \text{ volts}$$

$$V_p = 120 \text{ volts}$$

$$f = 60 \text{ Hz}$$

$$C = ?$$

$$R_L = ?$$

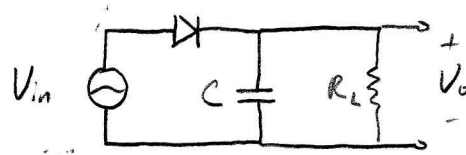

Small ripple is desired: $V_r \rightarrow 0$

Worst case: $V_r = 5 \text{ volts}$

$$V_r = \frac{V_p}{f C R_L}, \quad \text{assuming } R_L = 10 \text{ k}\Omega$$

↑ prototyping only!


$$5 = \frac{120}{60(C)(10000)}$$

$$C = 0.00004 \text{ F} = 40 \mu\text{F}$$

* increase C will result in smaller ripple

* Design #2 - Full wave rectifier

* Designing Power LED:

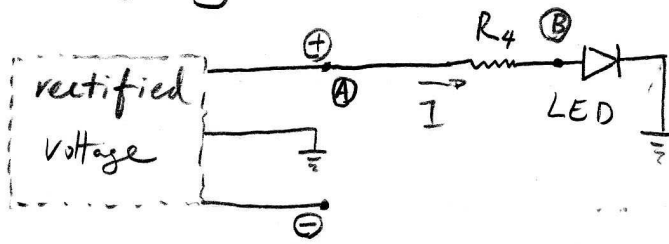

- The rectified positive voltage is 52 volts, this means node A is 52 volts $\rightarrow V_A = 52$ volts
- From data sheet, under normal operation, the LED has a voltage drop of 3.7 volts, and continuous current of 10.28×10^3 mA.

calculating of R_4 :

$$\frac{V_A - V_B}{R_4} = I$$

$$V_A = 52 \text{ volts}$$

$$V_B = 3.7 \text{ volts}$$

$$I = 10.28 \times 10^3 \text{ mA}$$

$$\frac{52 - 3.7}{R_4} = 10.28 \times 10^3 \text{ mA}$$

$$R_4 = 4.7 \Omega$$

* A 4.7Ω resistor should be able to keep the power LED from damaging.