

**PLEASE READ:** The purpose of this document is to provide examples of pre-lab tasks. The designs, calculations, values, and any other technical aspects of this document will not be suitable for your design.


### ⊕ Important - rectifier design

1. Current handling of the diode


2. Peak inverse voltage (PIV)

= select a diode that has a reverse breakdown voltage at least 50% greater than expected PIV."

### ⊕ Design #1 - half wave rectifier

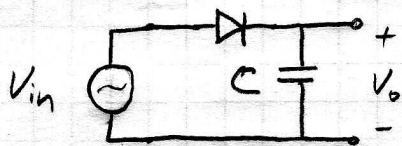

How it operates:

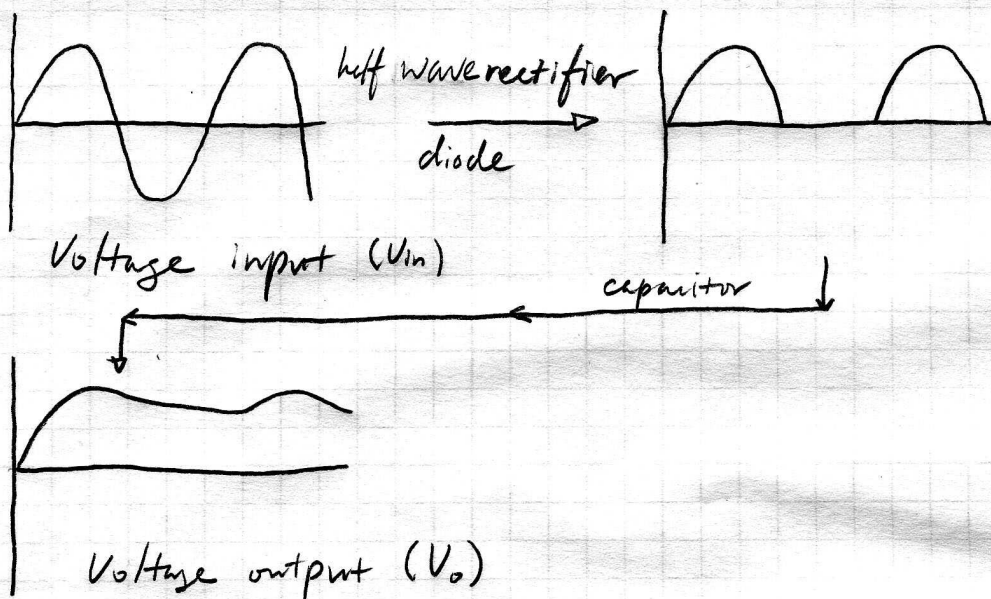

half wave rectifier ripple is given by:

$$V_r = \frac{V_p}{fCR_L}$$

$V_r$  = ripple voltage

$V_p$  = peak voltage

$f$  = frequency

$C$  = capacitance

Given design Spec:


$$V_r < 5 \text{ volts}$$

$$V_p = 120 \text{ volts}$$

$$f = 60 \text{ Hz}$$

$$C = ?$$

$$R_L = ?$$

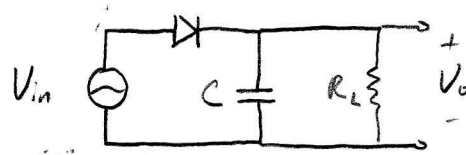

Small ripple is desired:  $V_r \rightarrow 0$

Worst case:  $V_r = 5 \text{ volts}$

$$V_r = \frac{V_p}{f C R_L}, \quad \text{assuming } R_L = 10 \text{ k}\Omega$$

↑ prototyping only!


$$5 = \frac{120}{60(C)(10000)}$$

$$C = 0.00004 \text{ F} = 40 \mu\text{F}$$

\* increase C will result in smaller ripple

\* Design #2 - Full wave rectifier

## ⊕ Designing Power LED:

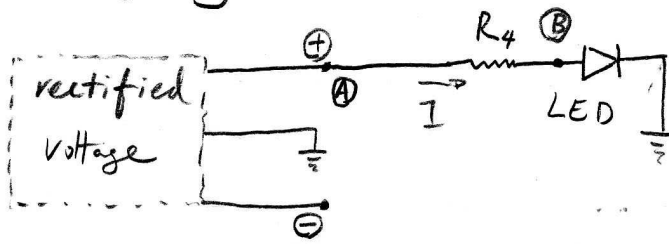

- The rectified positive voltage is 52 volts, this means node A is 52 volts  $\rightarrow V_A = 52$  volts
- From data sheet, under normal operation, the LED has a voltage drop of 3.7 volts, and continuous current of  $10.28 \times 10^3$  mA.

calculating of  $R_4$ :

$$\frac{V_A - V_B}{R_4} = I$$

$$V_A = 52 \text{ volts}$$

$$V_B = 3.7 \text{ volts}$$

$$I = 10.28 \times 10^3 \text{ mA}$$

$$\frac{52 - 3.7}{R_4} = 10.28 \times 10^3 \text{ mA}$$

$$R_4 = 4.7 \Omega$$

\* A  $4.7 \Omega$  resistor should be able to keep the power LED from damaging.